

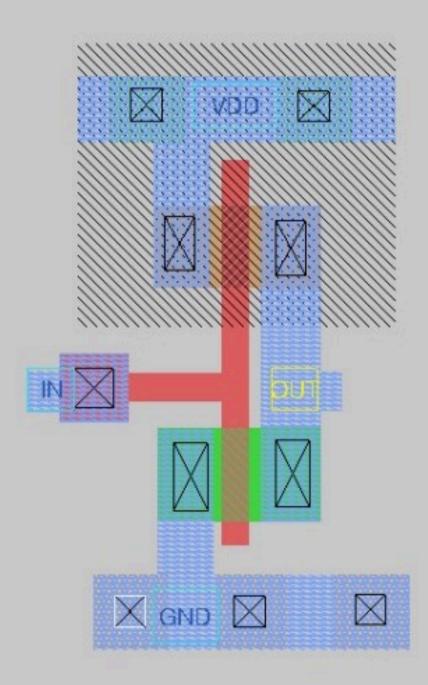
yers Drc Options DRC Loaded: INV Editing: INV Tool: box Technology: sky130A



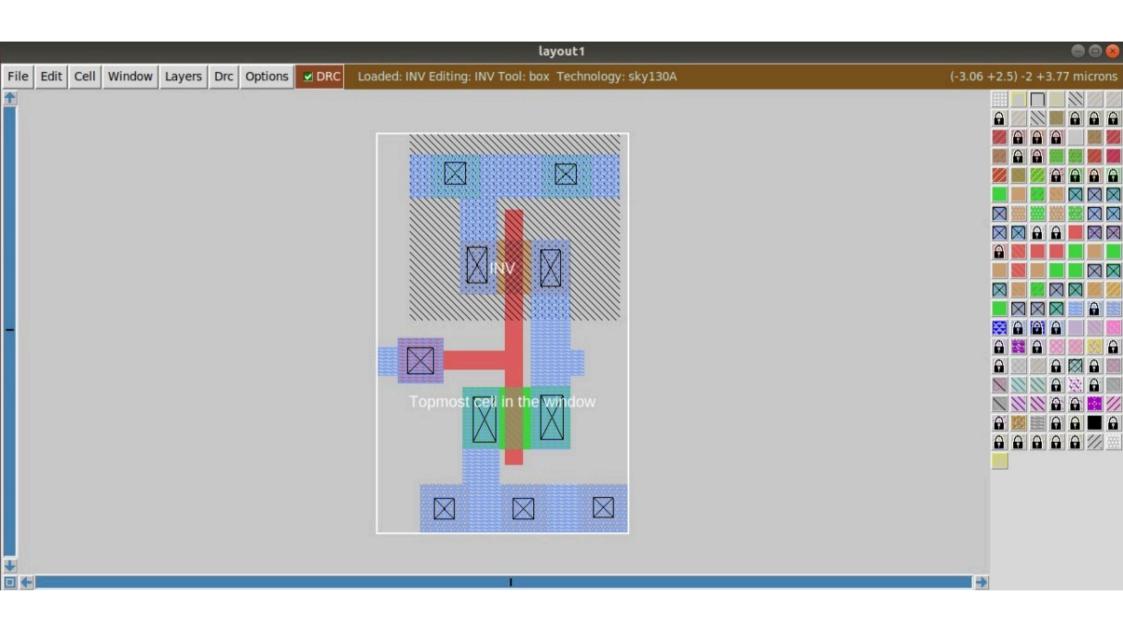

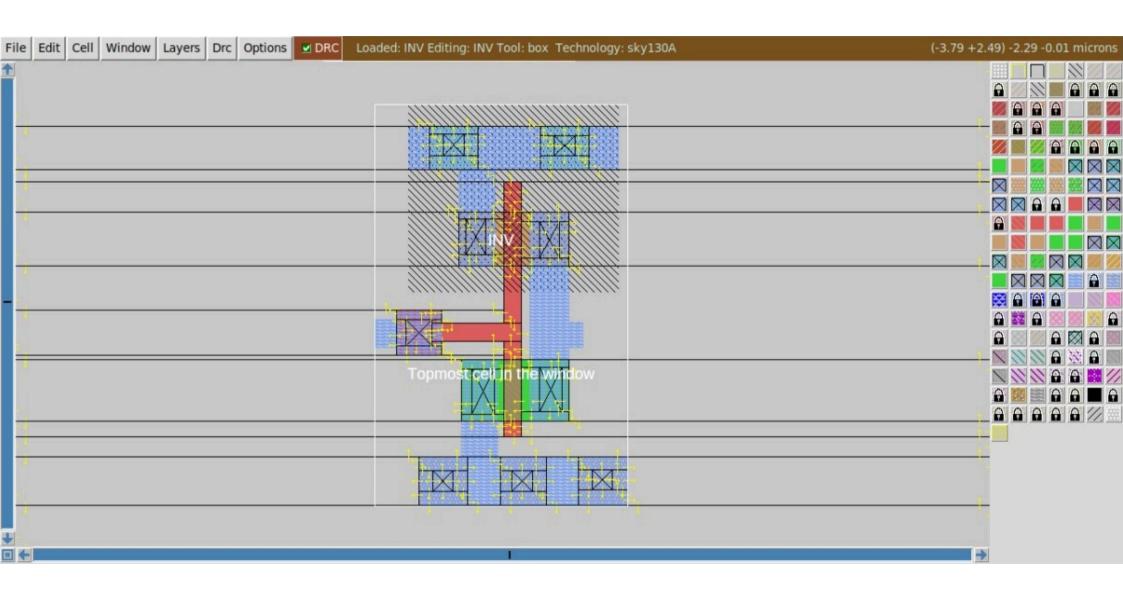

```
*INV.spice
 Open ▼
          ∄
 1 * SPICE3 file created from INV.ext - technology: sky130A
 3 .option scale=10m
5 .subckt INV IN VDD GND
6 X0 OUT IN VDD VDD sky130 fd pr pfet 01v8 ad=1.8n pd=0.17m as=1.71n ps=0.166m w=45 l=15
7 X1 OUT IN GND GND sky130 fd pr nfet 01v8 ad=2.08n pd=0.184m as=1.87n ps=0.176m w=52 l=15
8 CO IN VDD 0.0277f
9 C1 IN OUT 0.0418f
10 C2 VDD OUT 0.0897f
11 C3 IN GND 0.438f
12 C4 VDD GND 0.604f
13 C5 OUT GND 0.248f **FLOATING
14 .ends
15
16
17
18
```

```
1 * SPICE3 file created from INV.ext - technology: sky130A
 2
 3 .option scale=0.01u
 4 .include ./libs/pshort.lib
 5 .include ./libs/nshort.lib
7 //.subckt INV IN VDD GND
8 M1000 OUT IN VDD VDD pshort_model.0 ad=1800 pd=170 as=1710 ps=166 w=45 l=15
9 M1001 OUT IN GND GND nshort model.0 ad=2080 pd=184 as=1870 ps=176 w=52 l=15
10
11 VDD VDD 0 3.3V
12 VSS VSS 0 0V
13 Va IN VSS PULSE(0 3.3V 0 0.1ns 0.1ns 2ns 4ns)
14 CO IN VDD 0.0277f
15 C1 IN OUT 0.0418f
16 C2 VDD OUT 0.0897f
17 C3 IN GND 0.438f
18 C4 VDD GND 0.604f
19 C5 OUT GND 0.248f **FLOATING
20
21 //.ends
22 .tran 1n 20n
23 .control
24 run
25 .endc
26 .end
27
28
```

```
vsduser@vsdsquadron:~/Desktop/Std_cell/Inverter$ gedit INV.spice
vsduser@vsdsquadron:~/Desktop/Std_cell/InverterS ngspice INV.spice
** ngspice-27 : Circuit level simulation program
** The U. C. Berkeley CAD Group
** Copyright 1985-1994, Regents of the University of California.
** Please get your ngspice manual from http://ngspice.sourceforge.net/docs.html
** Please file your bug-reports at http://ngspice.sourceforge.net/bugrep.html
** Creation Date: Tue Dec 26 17:10:20 UTC 2017
Circuit: * spice3 file created from inv.ext - technology: sky130a
Scale set
Error on line 22:
c5 out 0 0.248f **floating
unknown parameter (*)
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Warning: va: no DC value, transient time 0 value used
Initial Transient Solution
Node
                                       Voltage
                                           3.3
out
in
                                             0
vdd
                                           3.3
VSS
                                             0
va#branch
                                             0
vss#branch
vdd#branch
                                   -3.3232e-12
```

No. of Data Rows : 150 ngspice 1 -> plot out vs time a

tran1: * spice3 file created from inv.ext - technology: sky130a

